

#100 DAYS OF RTL

DAY 4/100 Insights

MUX TREES

WITH SHANNON EXPANSION THEOREM

Understanding Shannon expansion Theorem

- Any Boolean function $f(w_1, w_2, \dots, w_n)$ can be written in the form

$$f(w_1, w_2, \dots, w_n) = \bar{w}_1 \cdot f(0, w_2, \dots, w_n) + w_1 \cdot f(1, w_2, \dots, w_n)$$

- or

$$f(w_1, w_2, \dots, w_n) = \bar{w}_1 \cdot f_{\bar{w}_1} + w_1 \cdot f_{w_1}$$

- where $f_{\bar{w}_1}$ is called the cofactor of f with respect to \bar{w}_1 and f_{w_1} is called the cofactor of f with respect to w_1
- Shannon's Expansion expresses a given logic function in terms of select inputs and data inputs required for logic synthesis using a multiplexer


Applications of Shannon Expansion


Reduce the power consumption in digital system

After synthesis, technology mapping and placement are complete, we apply Shannons expansion to the most critical sections of the circuit. This approach allows us to precompute the values of functions that depend on late-arriving critical signals and use a multiplexer to quickly select the appropriate value when the signal arrives. Any new logic elements created by this technique are incrementally placed in a minimally disruptive fashion to ensure convergence between the circuit optimization and the netlist placement.

It is very useful in Actel FPGAs

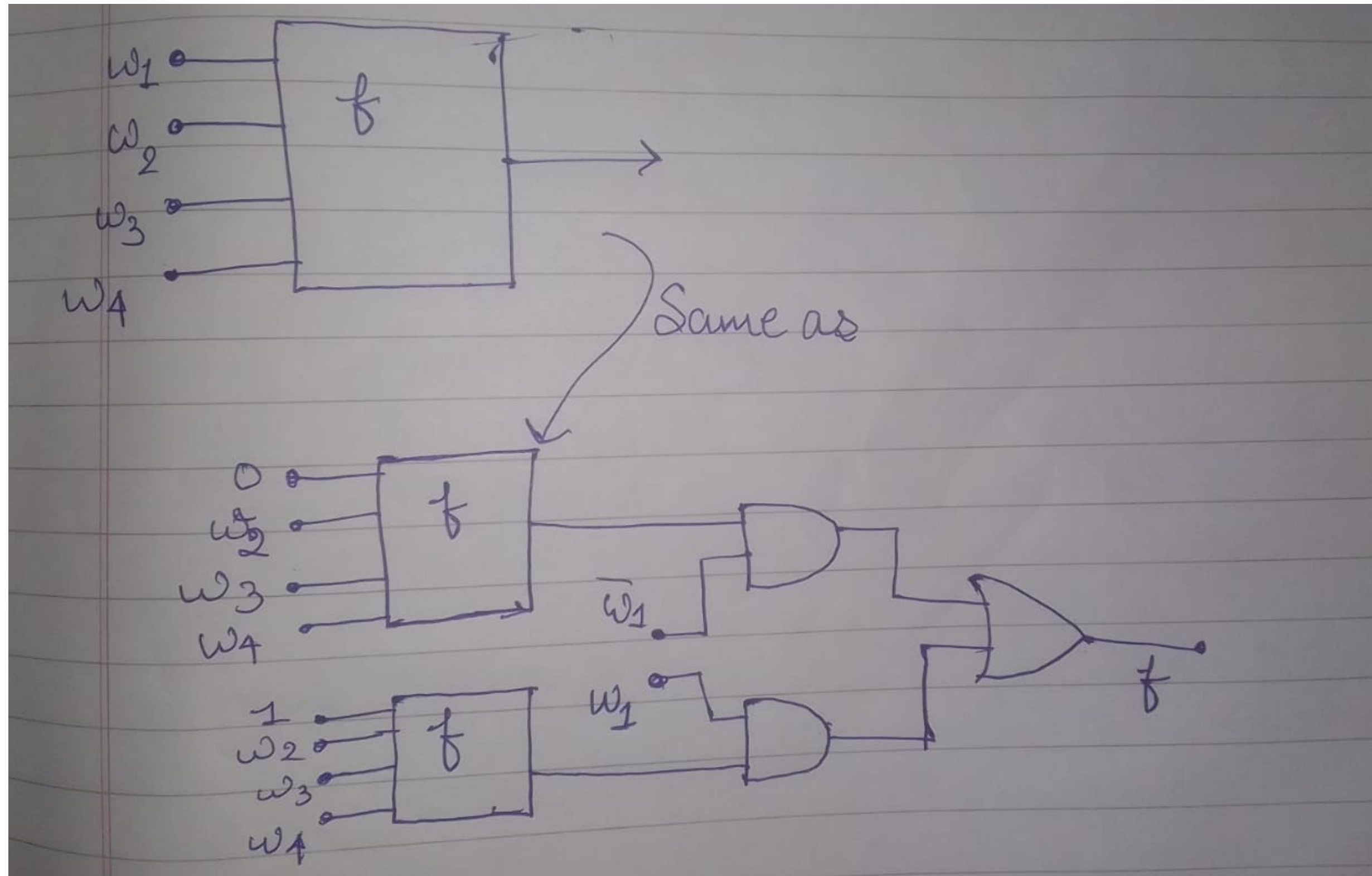Visual Representation of Shannon expansion theorem



 

(a) Graphical symbol

s_1	s_0	f
0	0	w_0
0	1	w_1
1	0	w_2
1	1	w_3


(b) Truth table

How we can use it to implement MUX TREE


$$Y = S_1' S_0' D_0 + S_1' S_0 D_1 + S_1 S_0' D_2 + S_1 S_0 D_3$$
$$= S_1' [0' S_0 D_0 + 0' S_0 D_1 + 0 S_0' D_2 + 0 S_0 D_3] +$$
$$S_1 [1' S_0' D_0 + 1 S_0 D_1 + 1 S_0' D_2 + 1 S_0 D_3]$$

$$= S_1' (S_0' D_0 + S_0 D_1) + S_1 (S_0' D_2 + S_0 D_3)$$

$$= S_1' F_0 + S_1 F_1$$

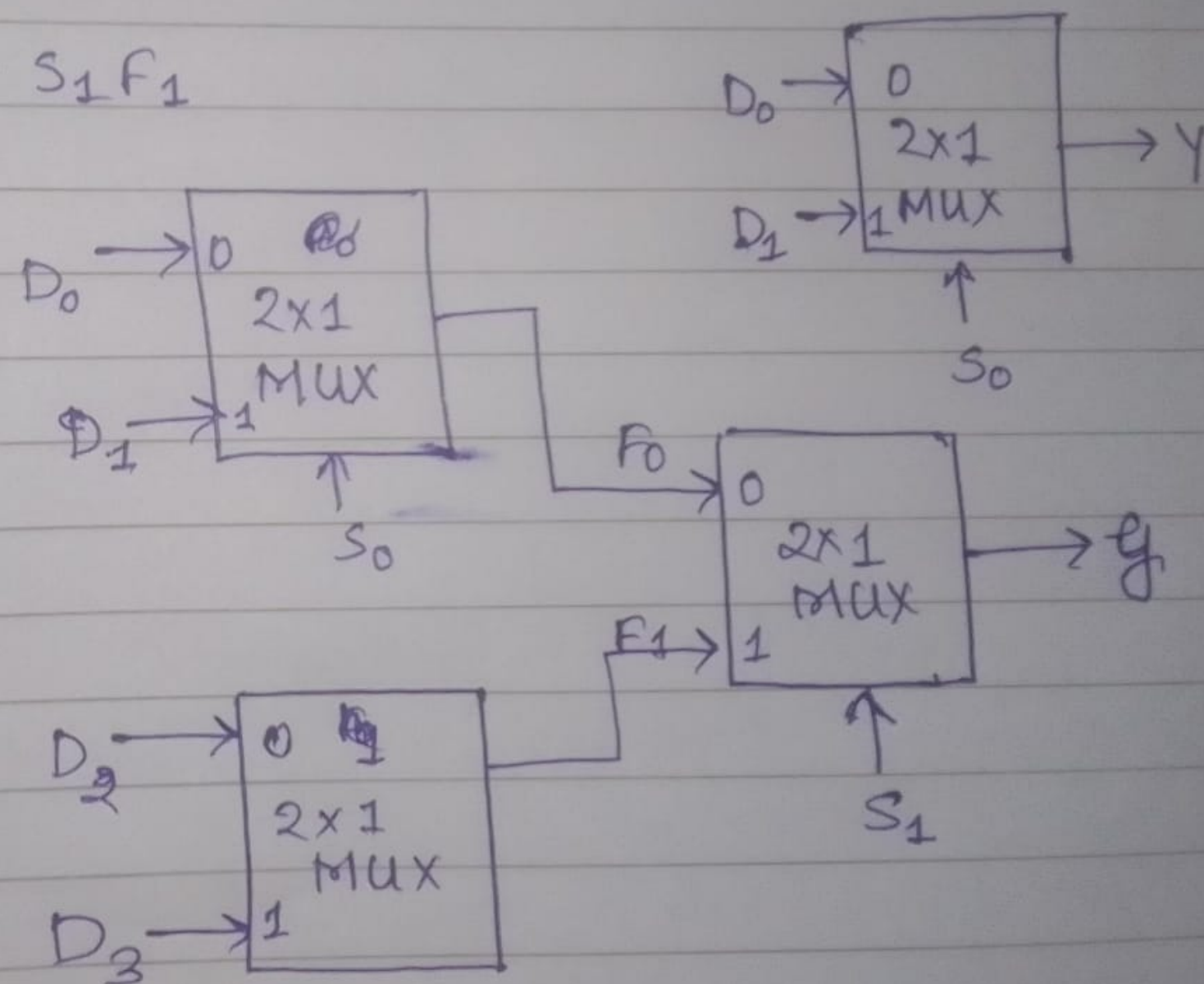

16X1 MUX using 4x1 MUX

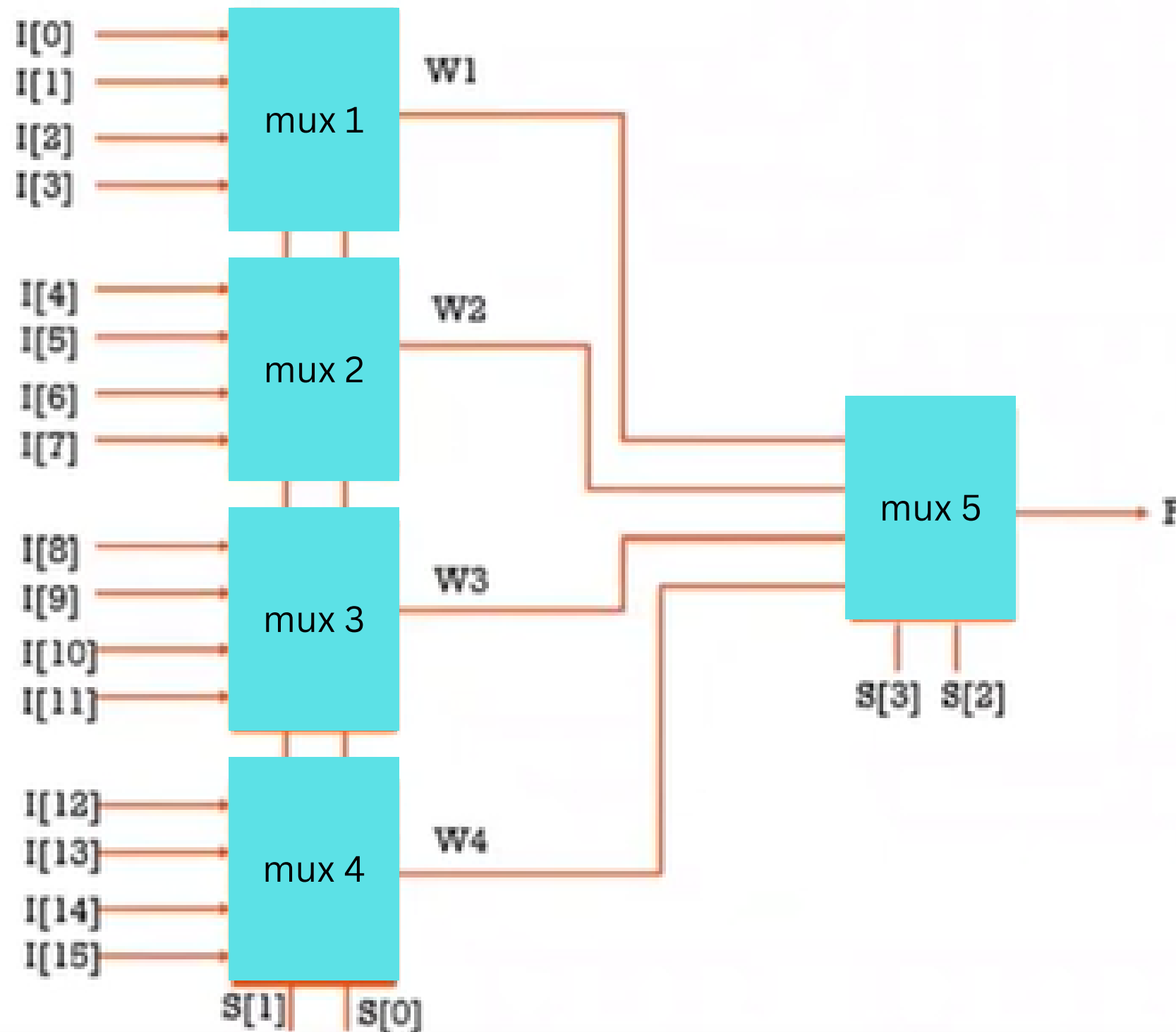


```

module mux16to1 (I, S, f);
input [0:15] I;
input [3:0] S;
output f;
wire [0:3] W;
mux4to1 Mux1 (I[0:3], S[1:0], W[0]);
mux4to1 Mux2 (I[4:7], S[1:0], W[1]);
mux4to1 Mux3 (I[8:11], S[1:0], W[2]);
mux4to1 Mux4 (I[12:15], S[1:0], W[3]);
mux4to1 Mux5 (W[0:3], S[3:2], f);
endmodule

module mux4to1 (W, S, f);
input [0:3] W;
input [1:0] S;
output reg f;
always @(*)
if (S == 2'b00)
f = W[0];
else if (S == 2'b01)
f = W[1];
else if (S == 2'b10)
f = W[2];
else
f = W[3];
endmodule
  
```

TEST BENCH

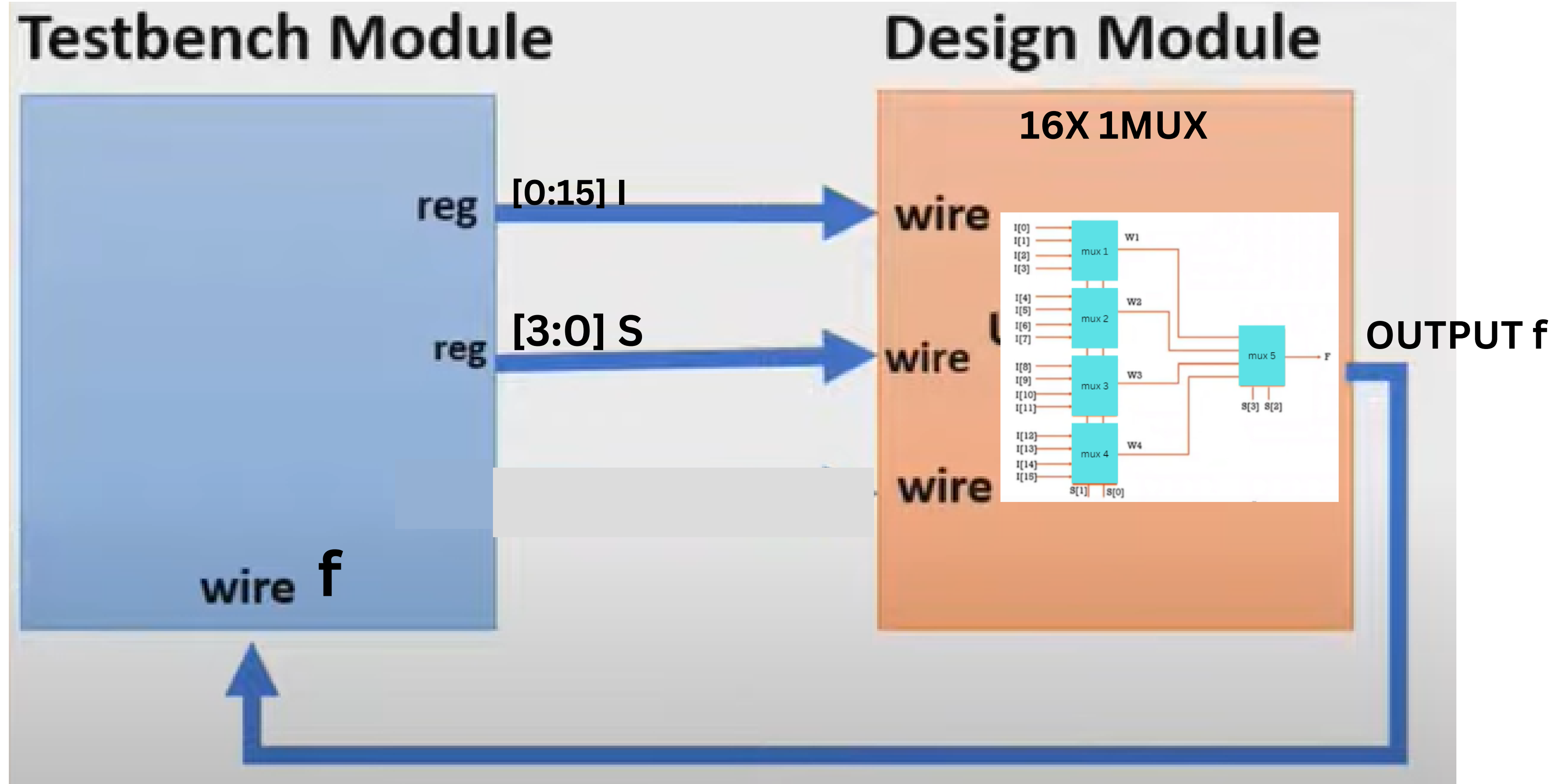


```
module mux_16_1_using_4_1_TB;
//inputs are reg
reg [15:0]i;
  reg [3:0]s;
//outputs are wires
wire f;
//instantiate UUT
mux16to1 mux16x1(.I(i),.S(s),.f(f));
  initial
  begin
    $monitor($time, "f=%b,i=%b,s=%b",f,i,s); //initialize inputs
    i=0;
s=0;
  end
always #5 i=i+1;
always #5 s = s +1;
endmodule
```


16x1MUXwith4x1MUX - [C:/Users/HP/Desktop/100daysofrt/DAY_4_MUX_TREE/16x1MUXwith4x1MUX/16x1MUXwith4x1MUX.xpr] - Vivado 2023.2

FileEditFlowToolsReportsWindowLayoutViewHelpQuick Access

Ready

Default Layout

Flow Navigator

PROJECT MANAGER

Settings

Add Sources

Language Templates

IP Catalog

IP INTEGRATOR

Create Block Design

Open Block Design

Generate Block Design

SIMULATION

Run Simulation

RTL ANALYSIS

Run Linter

Open Elaborated Design

Report Methodology

Report DRC

Report Noise

Schematic

SYNTHESIS

Run Synthesis

Open Synthesized Design

ELABORATED DESIGN - xc7a100tcsg324-2

SourcesNetlist

mux16to1

Nets (25)

Mux1 (mux4to1)

Mux2 (mux4to1)

Mux3 (mux4to1)

Mux4 (mux4to1)

Mux5 (mux4to1)

Source File Properties

Select an object to see properties

Project SummarySchematicmux16x1tb.vMUXTREE.v

5 Cells21 I/O Ports25 Nets

Mux1

S[3:0]

I[0:15]

S[1:0]

W[0:3]

f

mux4to1

Mux2

S[1:0]

W[0:3]

f

mux4to1

Mux3

S[1:0]

W[0:3]

f

mux4to1

Mux4

S[1:0]

W[0:3]

f

mux4to1

Mux5

S[1:0]

W[0:3]

f

mux4to1

Tcl ConsoleMessagesLogReportsDesign Runs

synth_1

constrs_1

Not started

impl_1

constrs_1

Not started

Type here to search

11:2130-11-2023